

N23272

B.E./B.TECH. DEGREE END SEMESTER EXAMINATIONS – NOV. 2023

First Semester

Computer Science and Engineering

23EE11C – Basic Electrical and Electronics Engineering

Regulations 2023

Time : Three hours

Maximum : 100 marks

Answer ALL Questions

Part A – (10 x 2 = 20 Marks)


1. Two resistances of 40Ω and 70Ω are connected in parallel across a 50V battery source feeding a constant current to the load. Compute the total current fed by the battery. CO1-K2
2. Draw a sinusoidal waveform and write the expression for rms value and average value. CO1-K1
3. State Faraday's laws of electromagnetic induction. CO2-K1
4. List the various applications of squirrel cage induction motor. CO2-K1
5. Name the various parts of induction type energy meter. CO3-K1
6. Distinguish between moving coil and moving iron instruments based on any two salient features. CO3-K2
7. Define the term PIV. CO4-K1

N23272

8. Write few applications of transistors. CO4-K2
9. Classify the types of batteries commonly used. CO5-K2
10. Sketch the circuit diagram of ELCB. CO5-K2


Part B – (5 X 16 = 80 Marks)

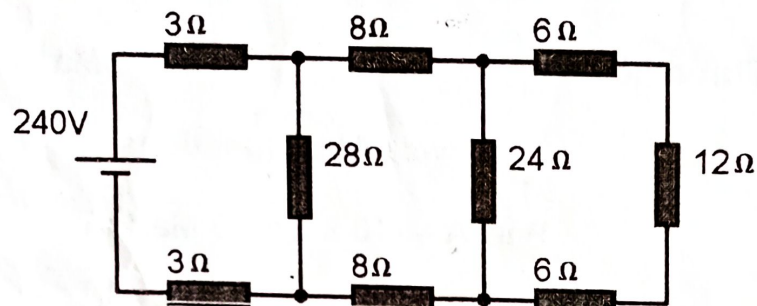11. (a) Determine the current in the 12 ohm resistance in the given circuit using Mesh current method, and also find the power dissipation across each element. CO1-K3 (16)



(Or)

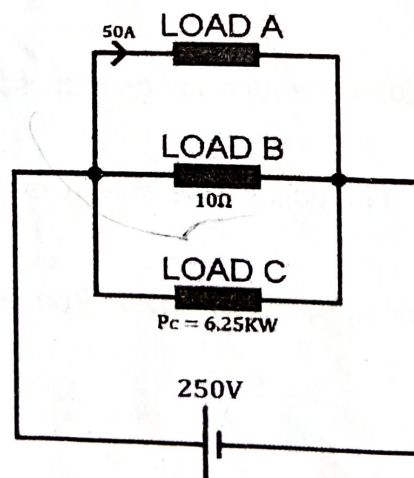- (b) Three loads A, B and C are connected in parallel across a 250 V source, Load A takes 50 A. Load B is a resistor of 10Ω and load C takes 6.25 kw. Calculate (i) load resistance A and B (ii) The currents through load B and C (iii) Power dissipation in loads A and B. CO1-K2 (16)



12. (a) (i) Derive the emf equation of a DC generator. CO2-K2 (8)
- (ii) A 4 pole, lap wound dc generator has a useful flux of 0.07 wb per pole. Armature consist of 440 conductors. Calculate the generated emf, when it is rotated at a speed of 900 r.p.m with a wind turbine. Also, calculate the generated emf if lap wound armature is replaced with wave wound armature. CO2-K3 (8)

(Or)

- (b) Explain the types of single-phase induction motor based on the starting mechanism with neat diagram. CO2-K2 (16)
13. (a) Explain the construction and working principle of a permanent magnet moving coil instrument with a neat diagram. CO3-K2 (16)

(Or)

- (b) (i) In detail, explain all the functions performed by multimeter and advantages of using a multimeter rather than analog meters. CO3-K2 (8)
- (ii) Explain the types of errors which occur while measuring using a measurement device. CO3-K1 (8)
14. (a) Describe the construction, operation and characteristic behavior of full wave rectifier constructed using p-n junction diode. CO4-K2 (16)

(Or)

- (b) (i) With a neat sketch, explain how n-p-n transistor can be used as switch in CE configuration. CO4-K2 (8)
- (ii) Summarize the differences between photo diode and LED. CO4-K2 (8)

15. (a) (i) Explain the necessity of earthing. Also, explain its types. CO5-K2 (8)
- (ii) Discuss with the help of basic block diagram of an Inverter used to convert DC to AC and also explain the working of the inverter. CO5-K2 (8)

(Or)

- (b) (i) Describe about electrical safety standards used in IT industry. CO5-K2 (8)
- (ii) Explain the construction and operation of Ni-Cd battery. Explain its advantages and disadvantages. CO5-K2 (8)
-